

Mechatronics System Integration (MCTA3203)

Week 7: PLC interfacing with microcontroller and PC over Ethernet/IP (ver 2.0)

Interfacing a PLC with a microcontroller and a PC over Ethernet/IP

Programmable Logic Controller (PLC) is a specialized industrial computer used for controlling and automating electromechanical processes in manufacturing plants, machinery, and various other applications. In this session, we shall use the OpenPLC Editor and interface it with a microcontroller. The OpenPLC Editor can be downloaded to your laptop/pc using the following link: <https://autonomylogic.com/>



Fig.1: OpenPLC Editor website

Example:


In this example, a basic ladder diagram consist of a single contact and coil on a rung will be created and simulated in the software and later uploaded onto the Arduino microcontroller. The ladder diagram representing the operation of a blinking led is as shown in the Fig. 2.



Fig. 2: Ladder diagram for blinking led

Create and Simulate the Ladder Diagram using OpenPLC Editor

1. Download OpenPLC Editor
2. Launch the software after downloading.
3. Start a new project (File → New → New Folder and name it →Select Folder)


4. Name the project: in the Create a new POU pop up window, name the project and select language → LD (ladder diagram)
5. Press “+” the to create new variable and name it. (Class Filter= local, Type = BOOL).
6. Start creating the Ladder Diagram by right clicking and choose Add.
7. Create the Left and the Right power rails, Contact (negated), Coil as shown in **Fig. 2**.
8. Once the ladder diagram is created, compile it by clicking the icon .
9. The blinking led simulation can now be seen in the editor.


Uploading and Testing the Ladder Diagram on Arduino

1. Associate the variables that have been created in the Ladder Diagram with the led pin on the Arduino board. You can check the associated pin between open PLC variables and various types of microcontrollers from the OpenPLC Editor website. On the Documentation menu, choose OpenPLC Runtime and then Physical Addressing. Refer to the correct microcontroller type and digital out pins.
2. For example, if using Arduino Mega board, and the led is connected to pin no. 14, the associated Digital Out pin on the OpenPLC Editor should be %QX0.0. This need to be typed into the Location of the variable in the editor.

Description:		Class Filter:	All					
#	Name	Class	Type	Location	Initial Value	Option	Documentation	
1	led	Local	BOOL					



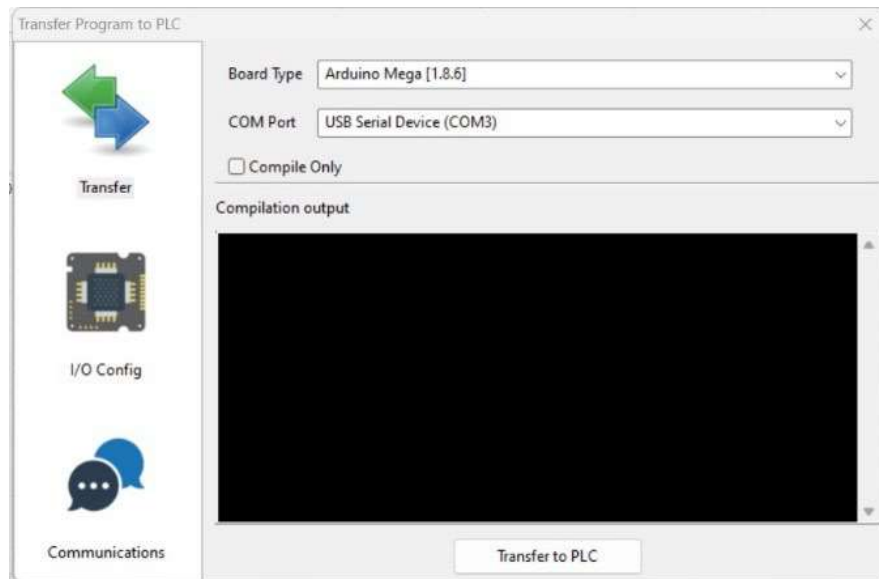3. Connect the Arduino board to your laptop and take note of the COM port number.
4. Once connected, compile the ladder diagram program to the Arduino board by clicking the icon . A window will pop up, select the correct board, type in the correct COM port number and proceed by pressing Transfer to PLC button.



5. The led should now be blinking according to the written ladder diagram program.

Exercise:

Modify the ladder diagram so that the blinking time interval of the led can be increased. For this exercise, you can use a timer block in the OpenPLC editor to control the led blinking time. Timer block (Right click, Add→Block→Standard function blocks→ Timers), Variable to input time delay (Right click, Add→Variable→Expression = T# xxx ms). Simulate this in OpenPLC Editor and transfer this modified ladder diagram program to your Arduino board.

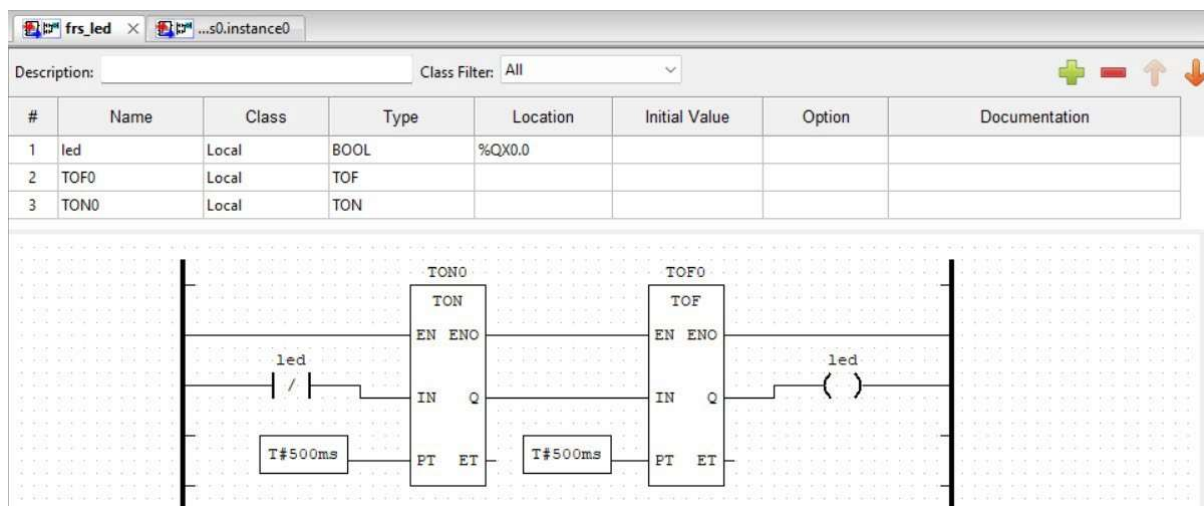


Fig. 3

Task

Start – Stop Control Circuit

Develop a Start-Stop Control Circuit by using ladder diagram created in OpenPLC, compile, simulate and transfer the ladder diagram program to Arduino Board. The circuit with pin configuration is shown in Fig. 4.

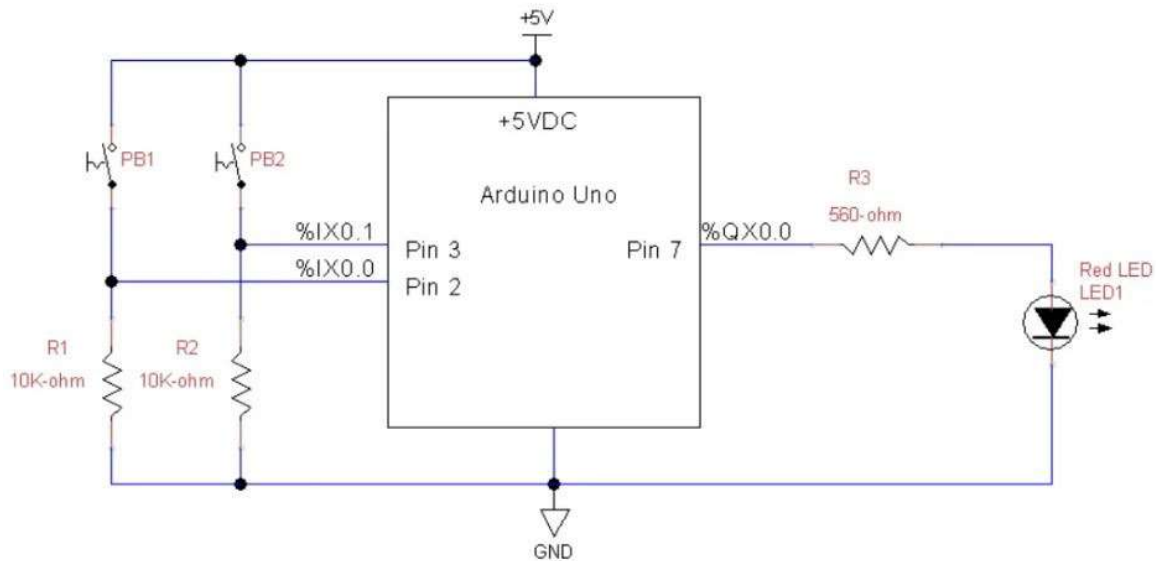


Fig. 4: Start-Stop Control Circuit

Required Hardware and Software:

- OpenPLC Editor software
- Arduino Board
- 2 Push Button Switches
- LED
- Resistors
- Jumper Wires
- Breadboard

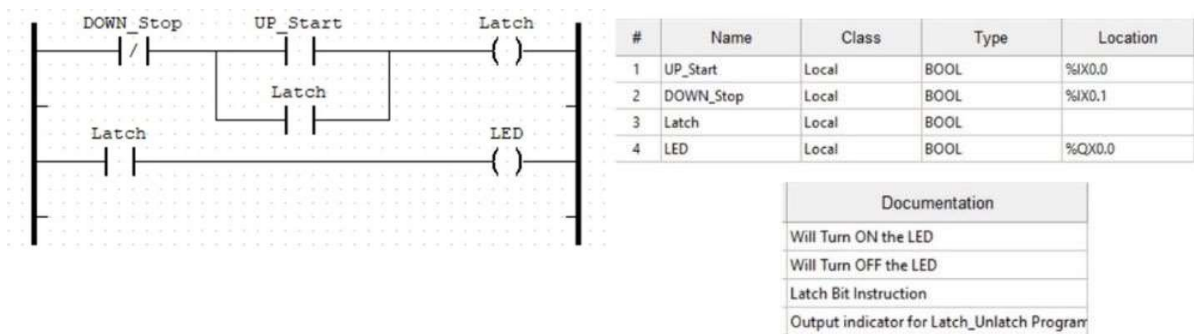


Fig. 5: Ladder Diagram for the Start-Stop Control Circuit

Experiment Steps:

1. Create the ladder diagram shown in **Fig. 5**.
2. Specify all variables used in the ladder diagram.
3. Compile and simulate the ladder diagram in OpenPLC Editor.
4. Upload the ladder diagram to the Arduino board.
5. Ensure to select correct COM port number and all pin association between the OpenPLC variables and Arduino board.
6. Build the circuit as shown in **Fig. 6**.
7. Test the functionality.

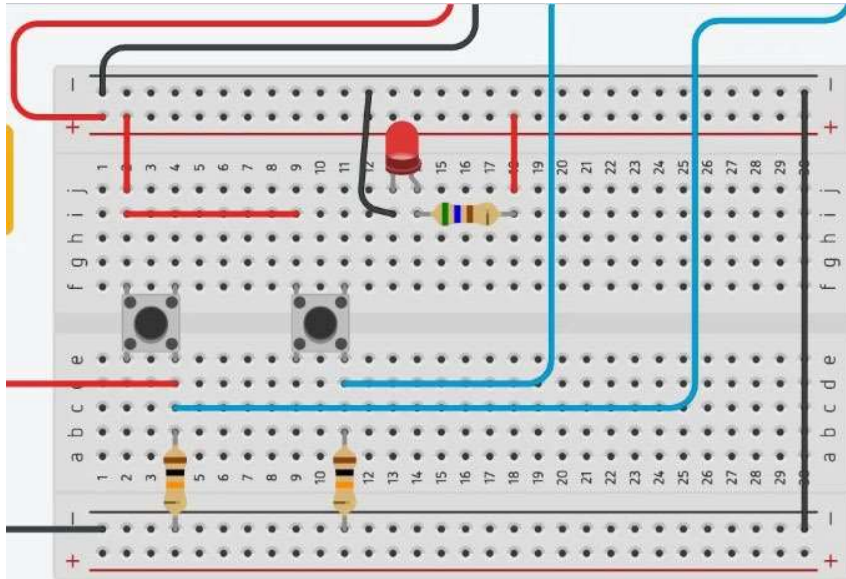


Fig. 6

References

- [1] <https://autonomylogic.com/>
- [2] <https://control.com/technical-articles/plc-ladder-logic-on-an-arduino-introduction-to-openplc/>
- [3] <https://control.com/technical-articles/plc-ladder-logic-on-an-arduino-building-a-start-stopcircuit/>